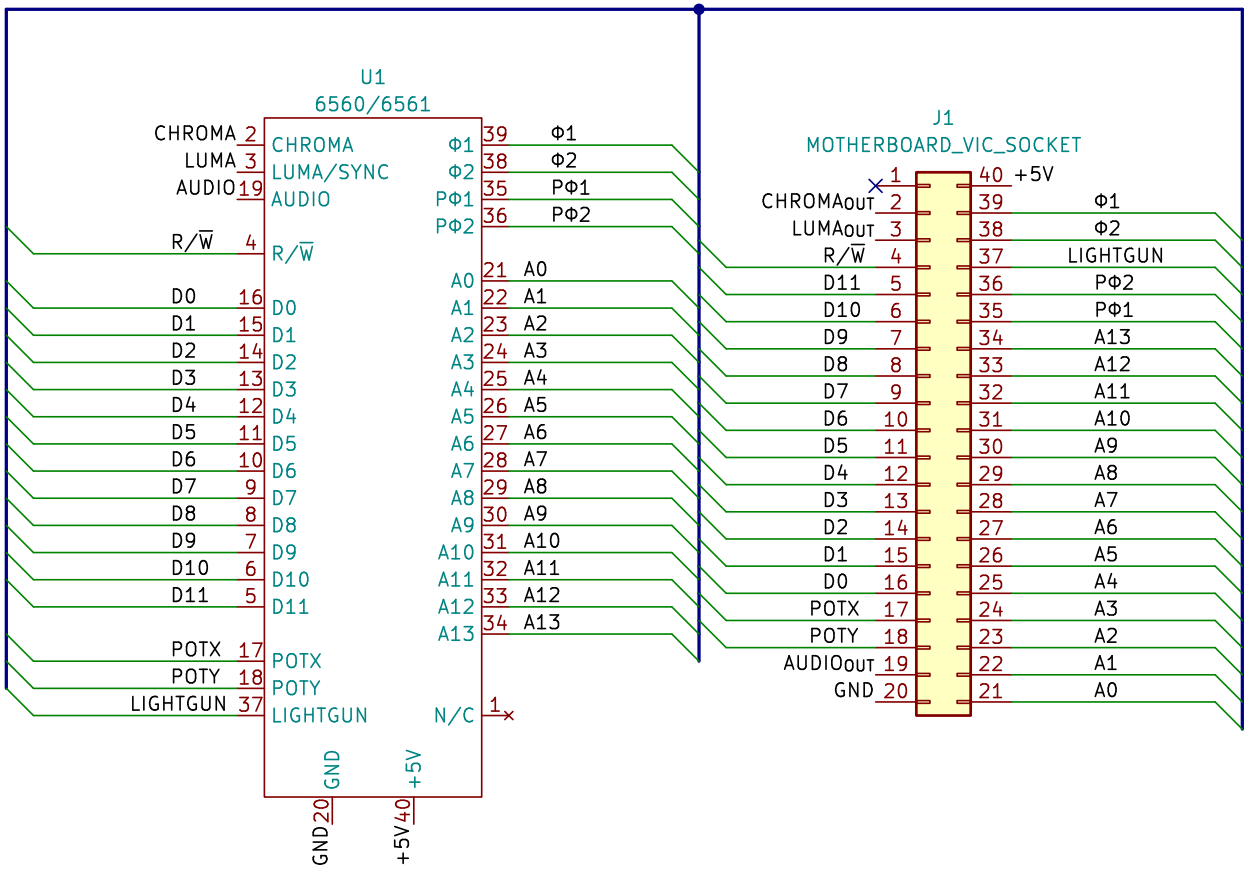

I've long been interested in trying to improve the VIC-20's rather poor video output quality.

Yes, I know there are replacement boards available, either for cost or for free, but I've not had much luck with those - I want to understand the problem and how it's fixed.

So I want to go "back to basics" ... start with the suggested circuit in the VIC 6560 datasheet.

The 6560 outputs essentially an S-Video signal, separated CHROMA and LUMA/SYNC. These can be used separately or passively combined to form a composite colour output.

Let's experiment with both.

Bridge the solder jumpers to passthrough the VIC output to the motherboard

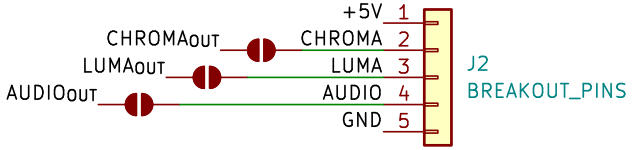

Brett Hallen

Sheet: /

File: VIC_6560_Breakout_RevB.kicad_sch

Title: Video Interface Chip (VIC) A/V Breakout Board

Size: A5	Date: 28/MAY/2026	**Rev: B**
KiCad E.D.A. 9.0.9		Id: 1/1